

Corso di Informatica 2 – Prof. Sciuto

# Flip-flops



Daniele Paolo Scarpazza  
Dipartimento di Elettronica e Informazione  
Politecnico di Milano


May 5th 2004

(sorry, 'english' is cheaper than 'italian with english terms')
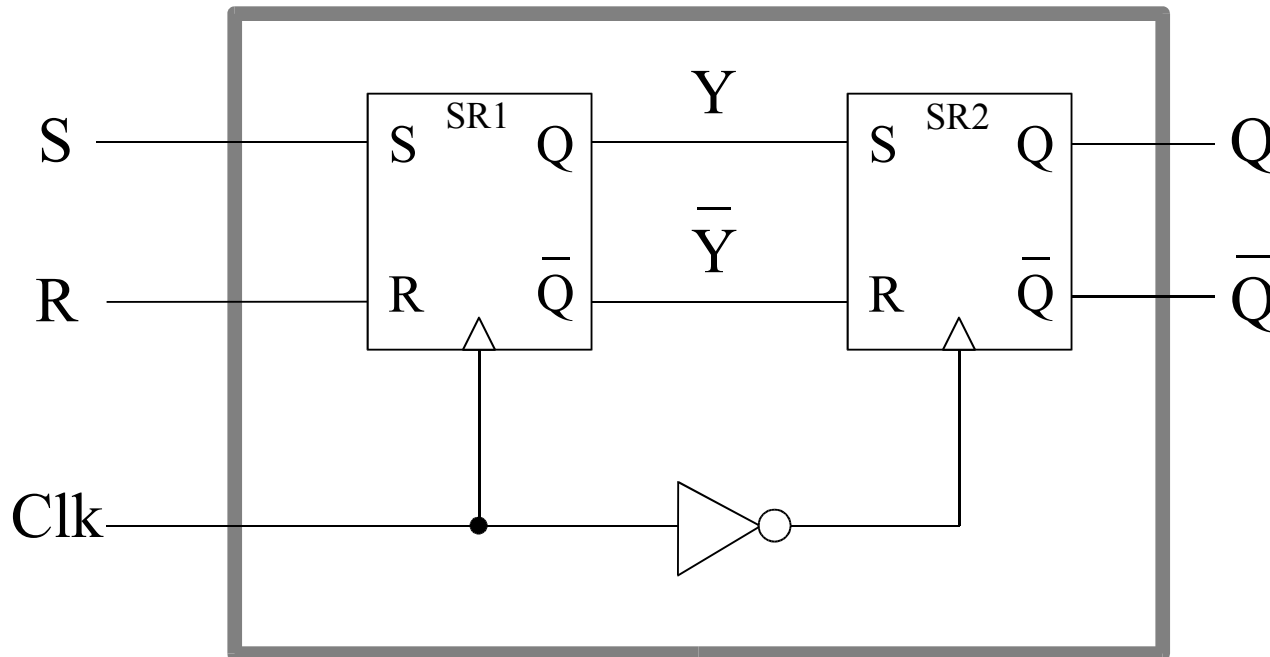
# The master-slave SR flip-flop

Structure: 2 SR synchronous latches;  
1 not gate;

Total cost: 4 nor + 4 and + 1 not  
(+1 not for D version)



# The master-slave SR flip-flop


Clock=1

SR1: transparent

S, R affect Y/!Y

SR2: opaque

Q/!Q are unaffected

 

# The master-slave SR flip-flop


Clock=0

SR1: opaque

S, R do NOT affect Y/!Y

SR2: transparent


Y/!Y affect Q/!Q

 
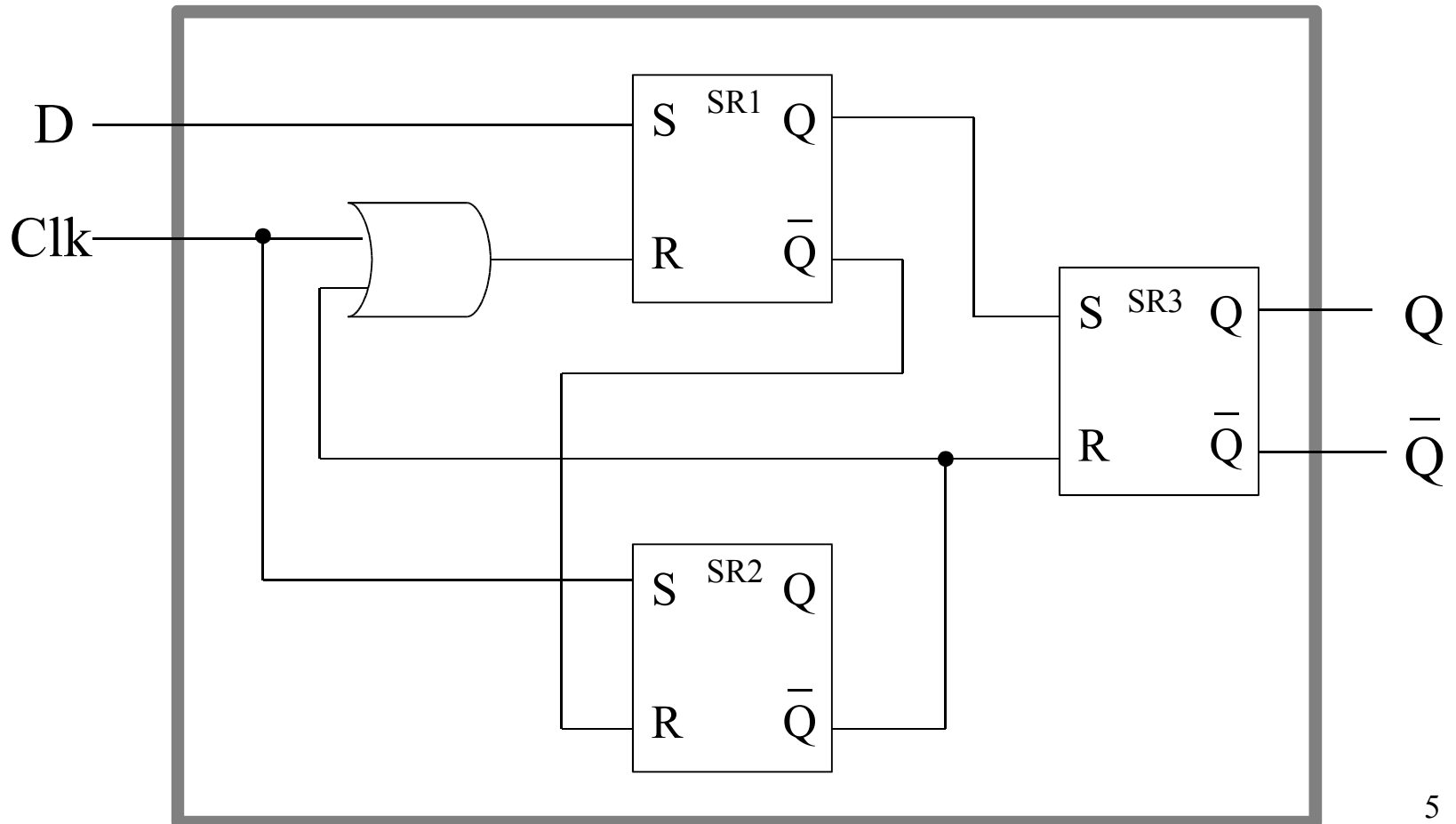
# The edge-triggered D flip-flop


Structure: 3 SR asynchronous latches;  
1 or gate;

Total cost: 6 nor + 1 or (cheaper than master-slave!)


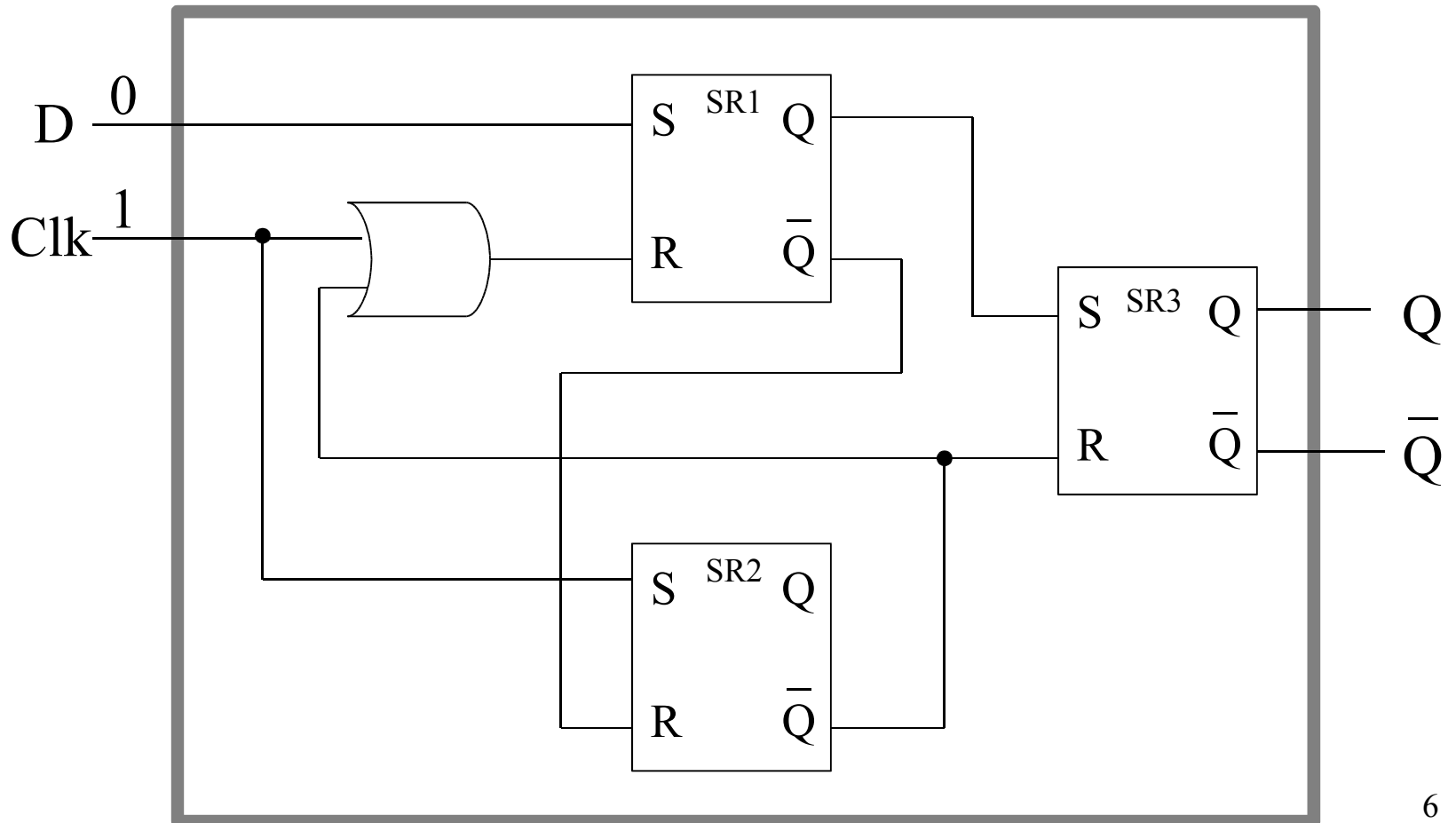
# The edge-triggered D flip-flop

Case 0:      Clock = 1  
              Data = 0



# The edge-triggered D flip-flop


Case 0:

Clock = 1

Data = 0

SR1: valid, 0 SR3: unaffected

SR2: invalid (prev state)

 


# The edge-triggered D flip-flop

Case 0+: Clock = 0

SR1: prev, 0 SR3: reset

Clock down Data = 0


SR2: reset

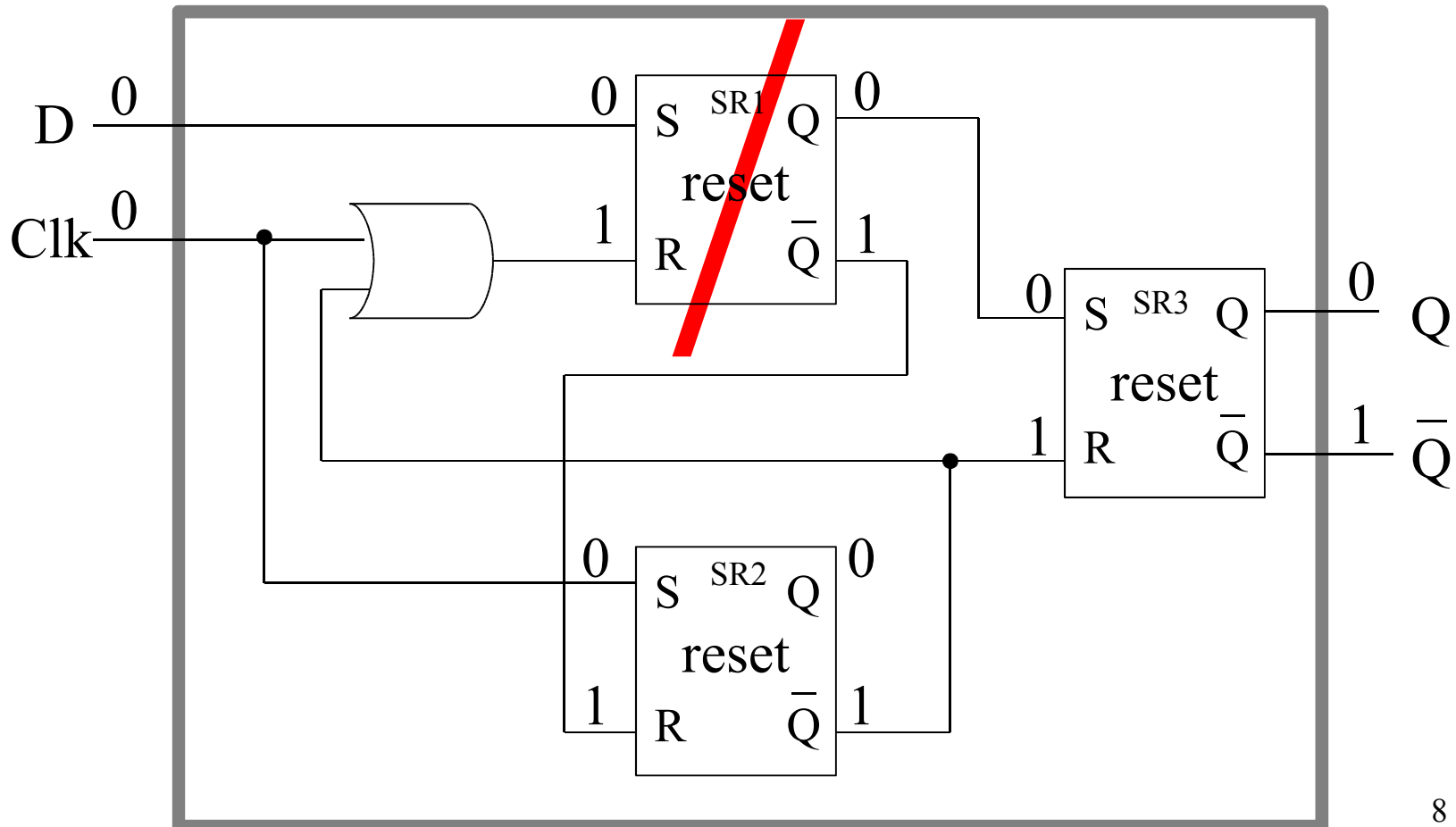


 
# The edge-triggered D flip-flop

Case 1:      Clock = 1  
              Data = 1



# The edge-triggered D flip-flop


Case 1:

Clock = 1

Data = 1

SR1: invalid SR3: unaffected

SR2: prev, 1 (prev state)

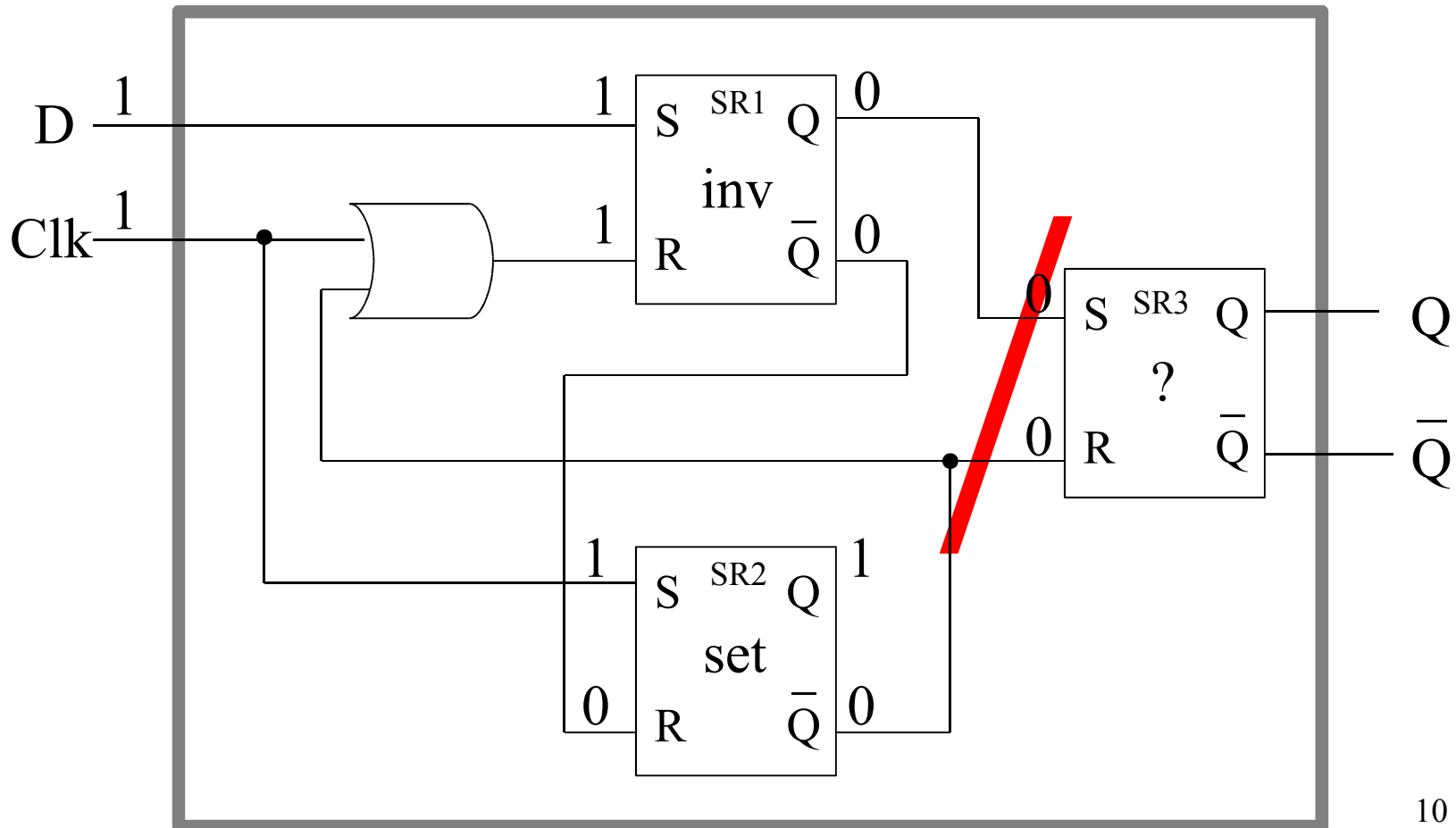


# The edge-triggered D flip-flop

Case 1+: Clock = 0

SR1: valid, 1 SR3: set


Clock down Data = 1

SR2: prev, 1

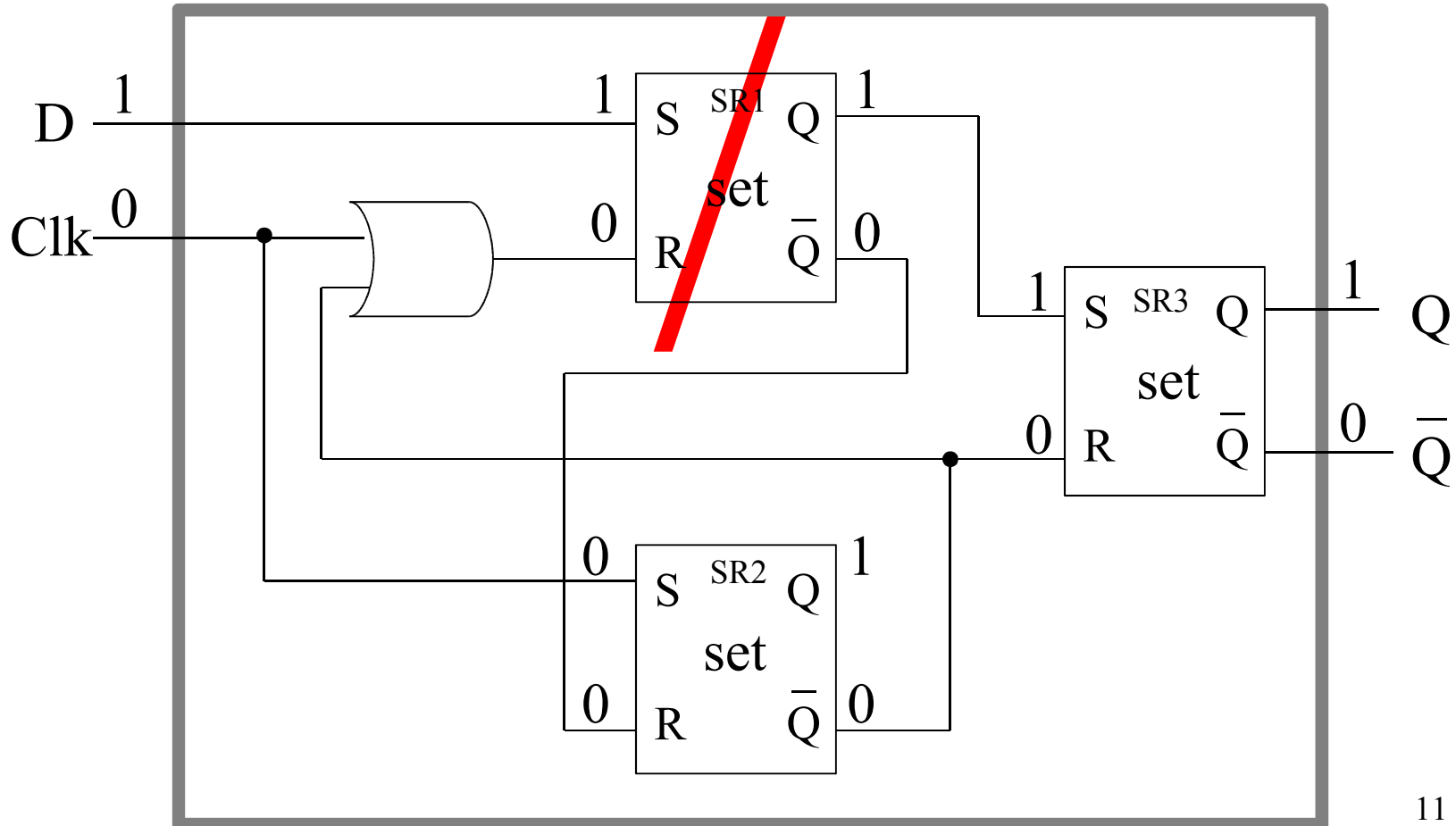


# Master-slave vs. edge-triggered

## Edge-triggered

 

## Master-slave

 

# Master-slave vs. edge-triggered: conclusions


The master-slave and the edge-triggered flip-flops  
are externally **IDENTICAL!**

Both sample the input signals at clock negative edge,  
and make it available at output.

Forget fig. 15, page 84.

# Do-it-yourself logic simulation

 1. Download MXE: “Modelsim Xilinx Edition” at:  
[www.xilinx.com/xlnx/xil\\_prodcat\\_product.jsp?title=modelsim\\_xe](http://www.xilinx.com/xlnx/xil_prodcat_product.jsp?title=modelsim_xe)
2. During installation request a free license;



3. Download  
scarpaz.vhd  
scarpaz.tcl  
and copy in dir:  
examples
4. Type:  
source scarpaz.tcl  
init  
  
dff  
dffet3