

Corso di Informatica 2 – Prof. Sciuto

Flip-flops




Daniele Paolo Scarpazza
Dipartimento di Elettronica e Informazione
Politecnico di Milano

May 5th 2004

The master-slave SR flip-flop

Structure: 2 SR synchronous latches;
1 not gate;

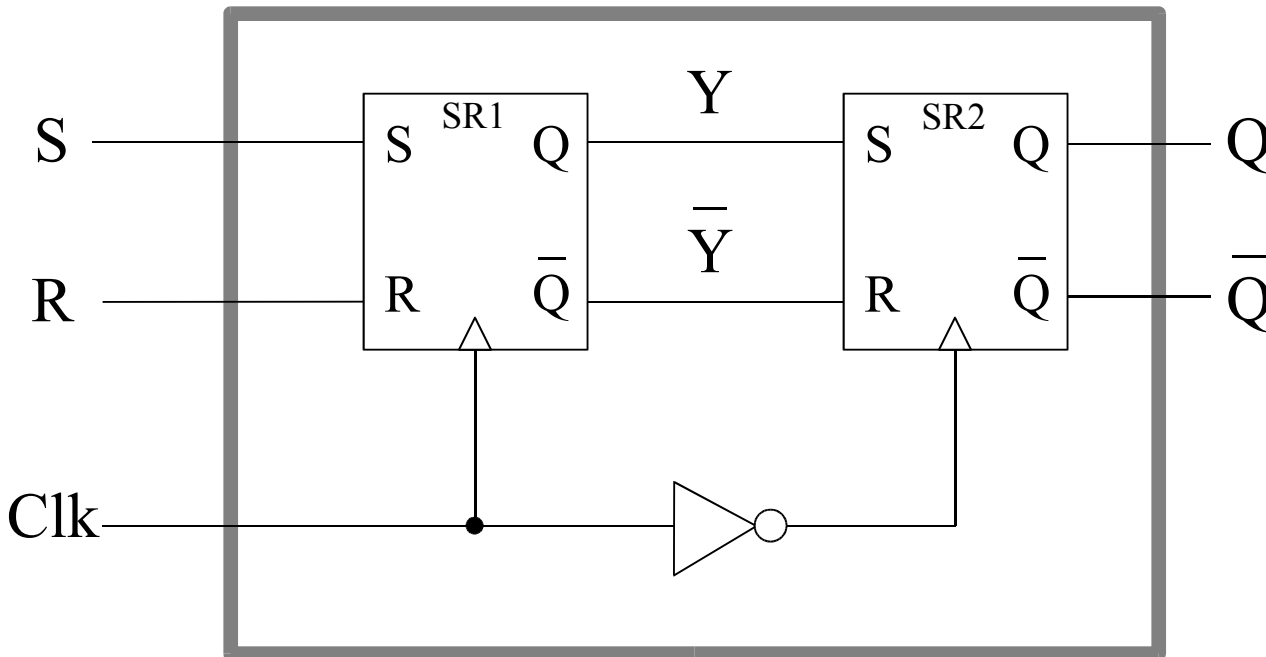Total cost: 4 nor + 4 and + 1 not
(+1 not for D version)



The master-slave SR flip-flop


Clock=1

SR1: transparent

S, R affect Y/!Y

SR2: opaque

Q/!Q are unaffected

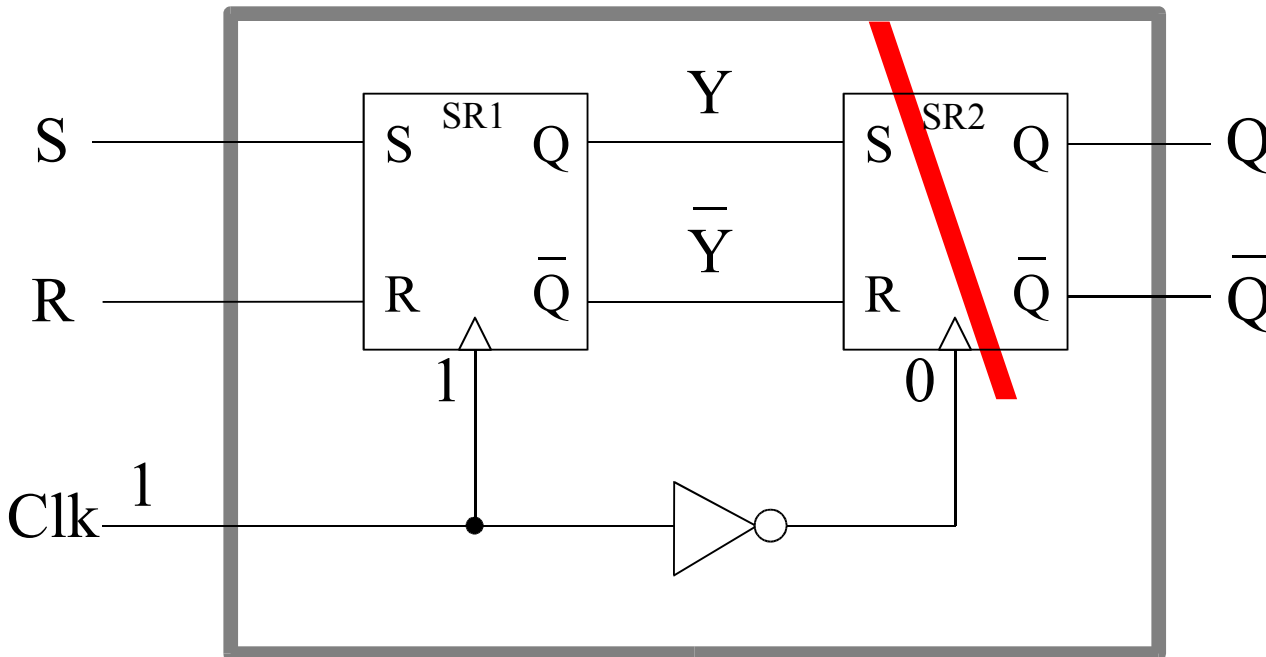

The master-slave SR flip-flop


Clock=0

SR1: opaque

S, R do NOT affect Y/!Y

SR2: transparent


Y/!Y affect Q/!Q

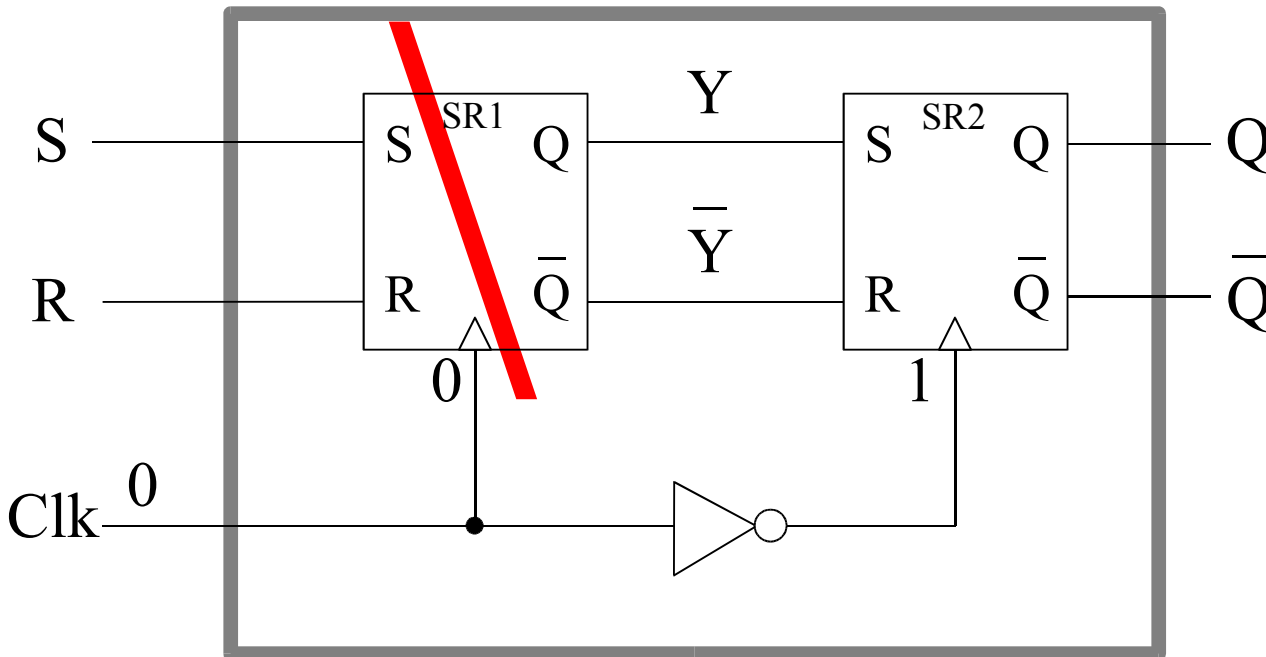

The edge-triggered D flip-flop


Structure: 3 SR asynchronous latches;
1 or gate;

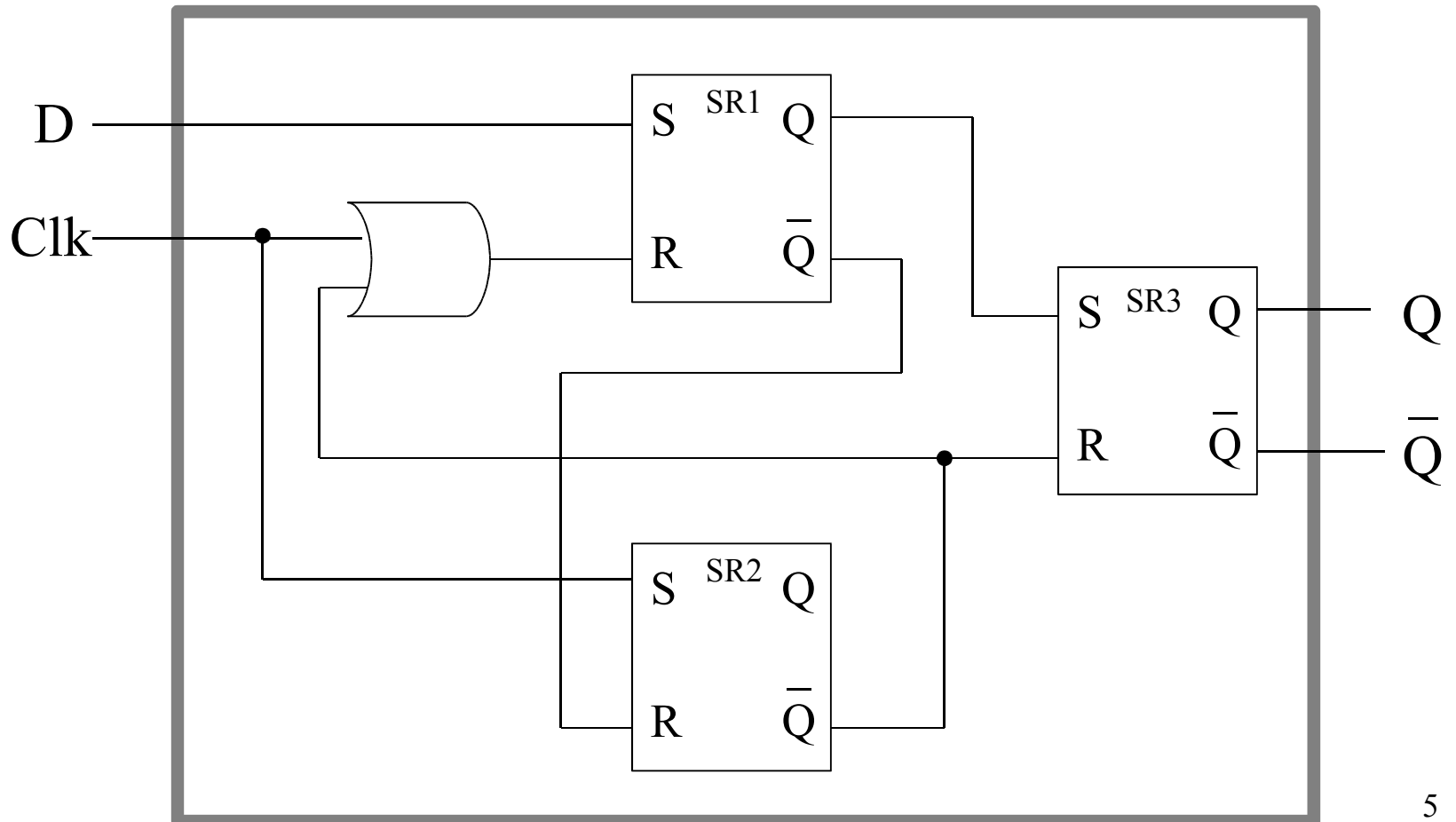Total cost: 6 nor + 1 or (cheaper than master-slave!)



The edge-triggered D flip-flop

Case 0: Clock = 1
 Data = 0

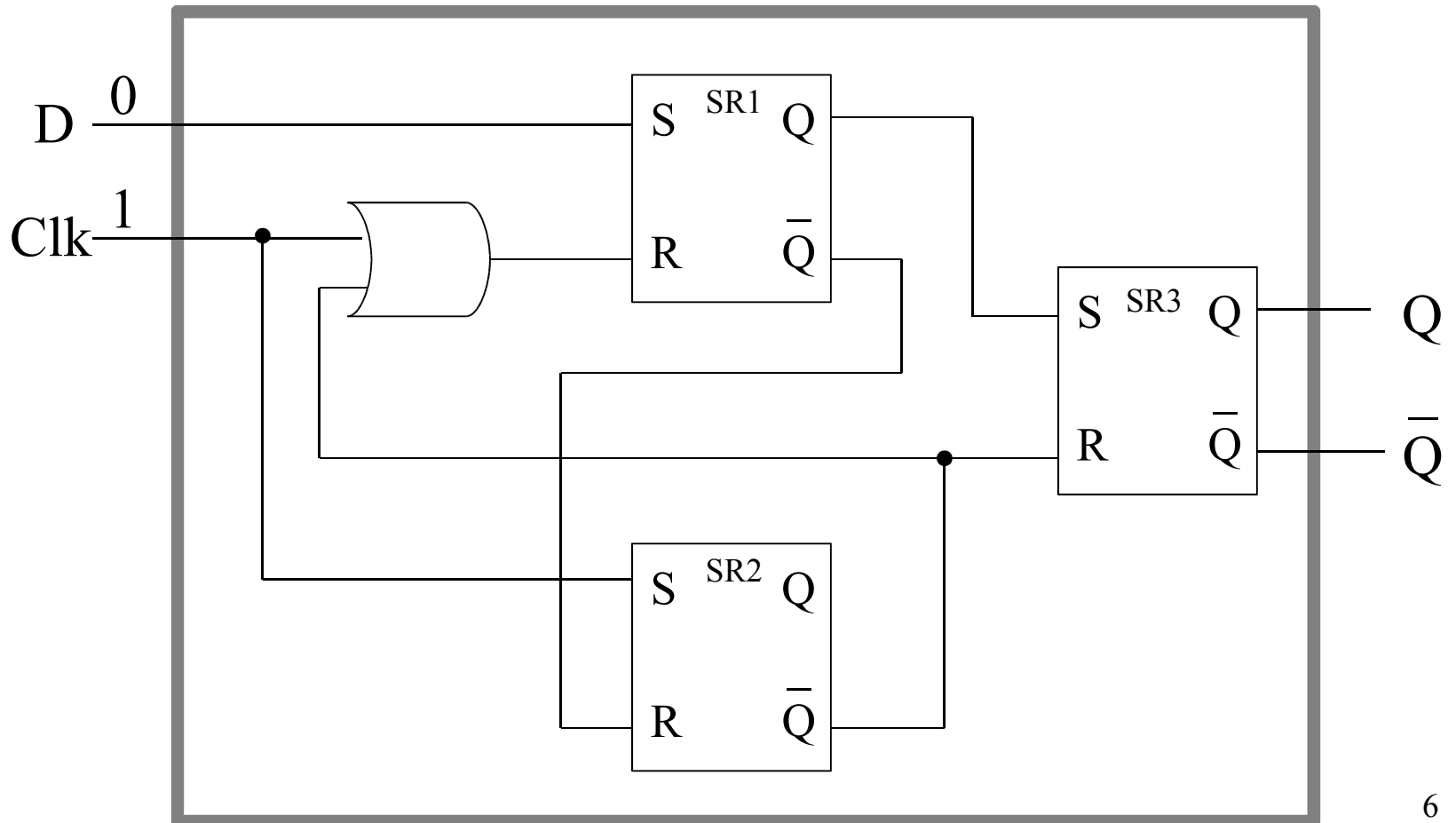

The edge-triggered D flip-flop


Case 0:

Clock = 1

Data = 0

SR1: valid, 0 SR3: unaffected

SR2: invalid (prev state)

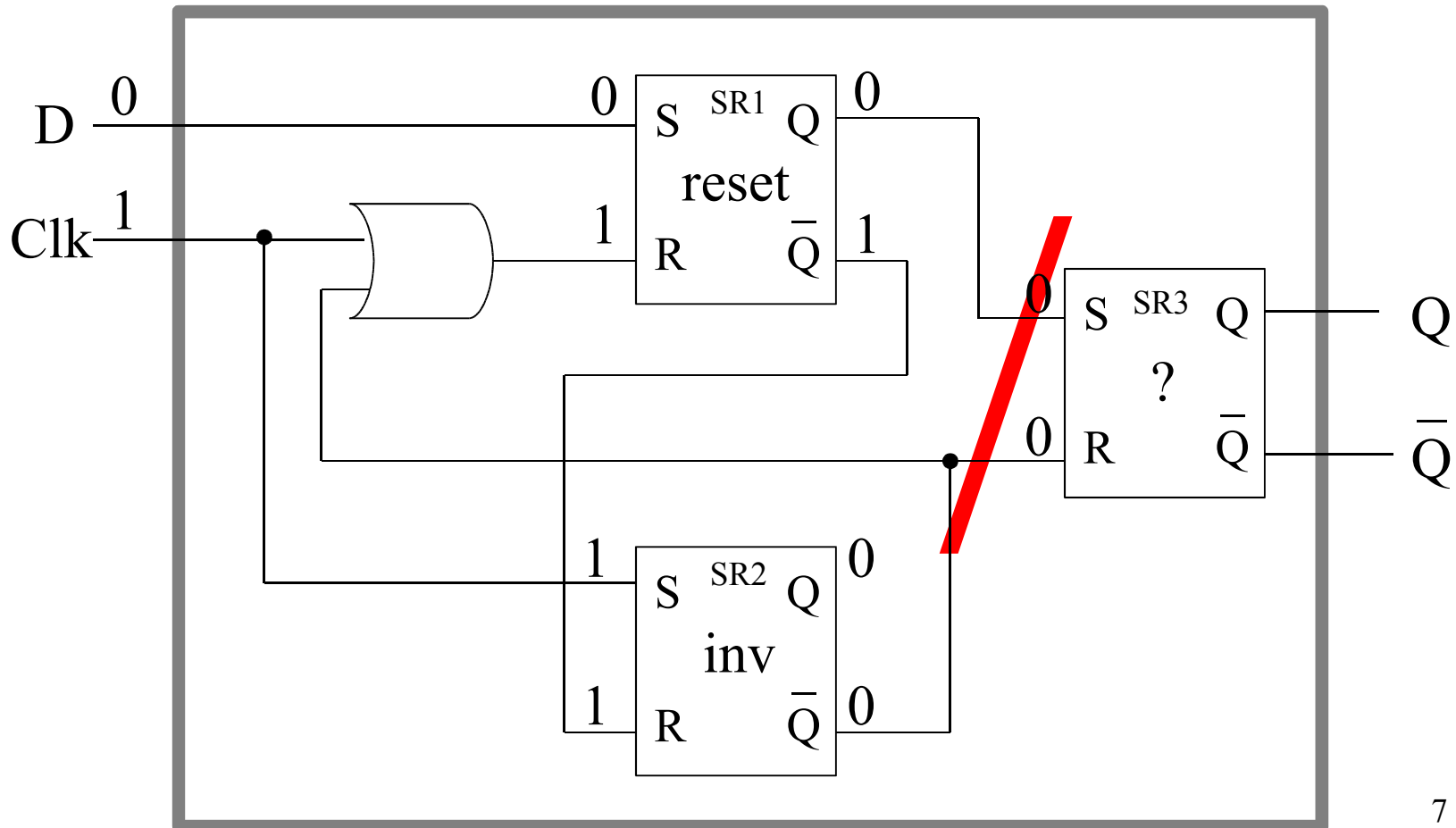


The edge-triggered D flip-flop

Case 0+: Clock = 0

SR1: prev, 0 SR3: reset


Clock down Data = 0

SR2: reset

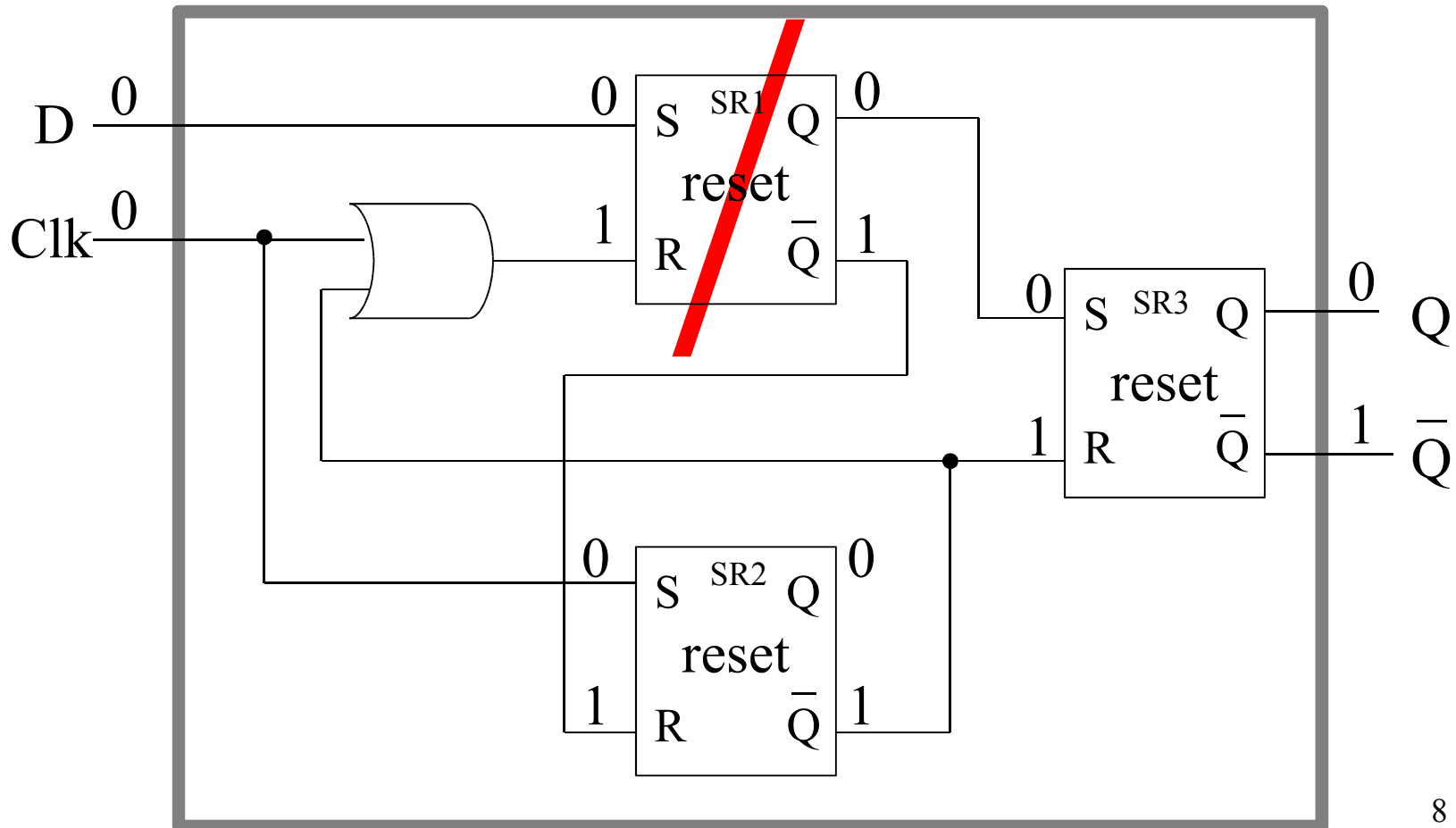

The edge-triggered D flip-flop

Case 1: Clock = 1
 Data = 1

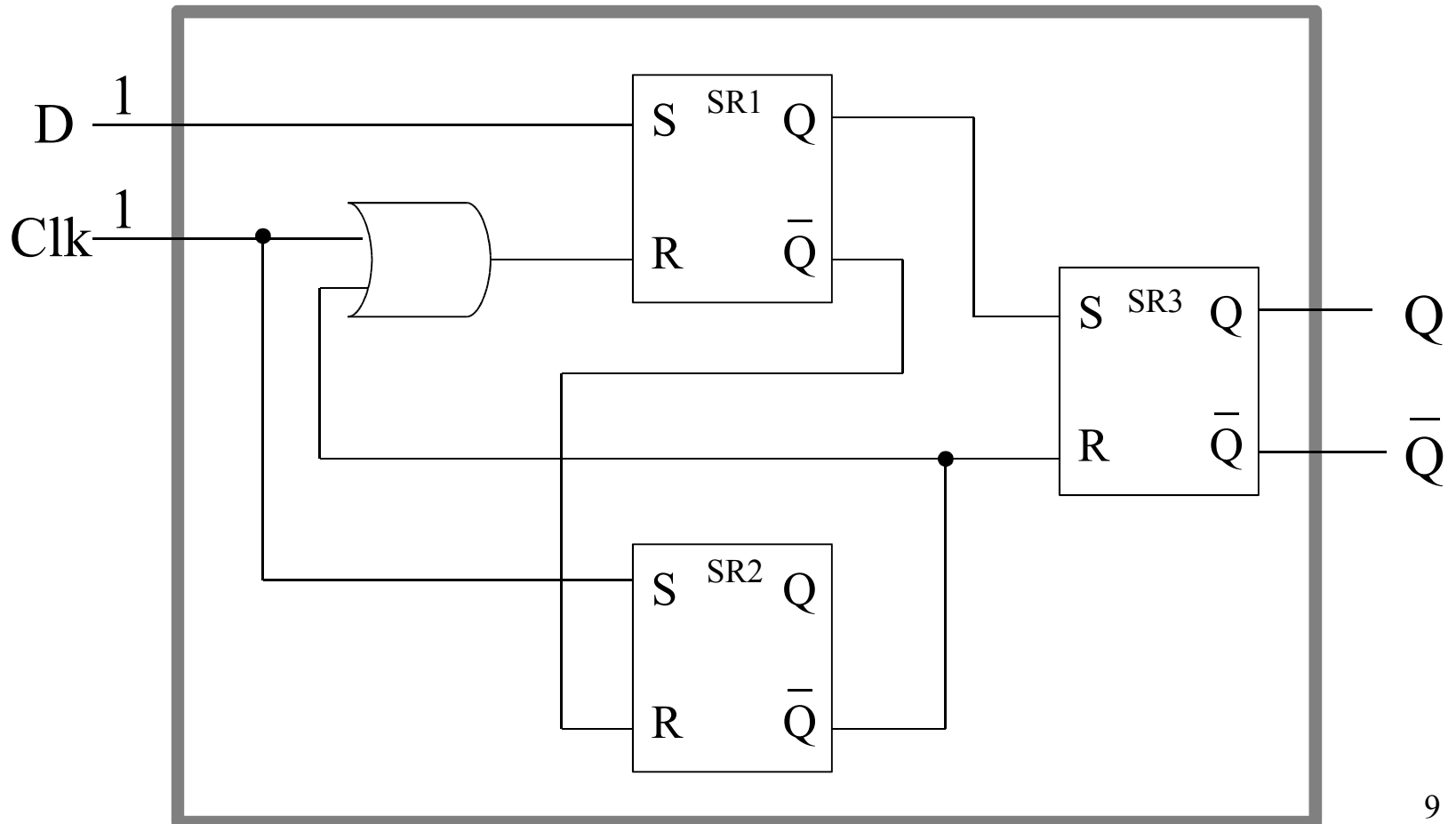

The edge-triggered D flip-flop


Case 1:

Clock = 1

Data = 1

SR1: invalid SR3: unaffected

SR2: prev, 1 (prev state)

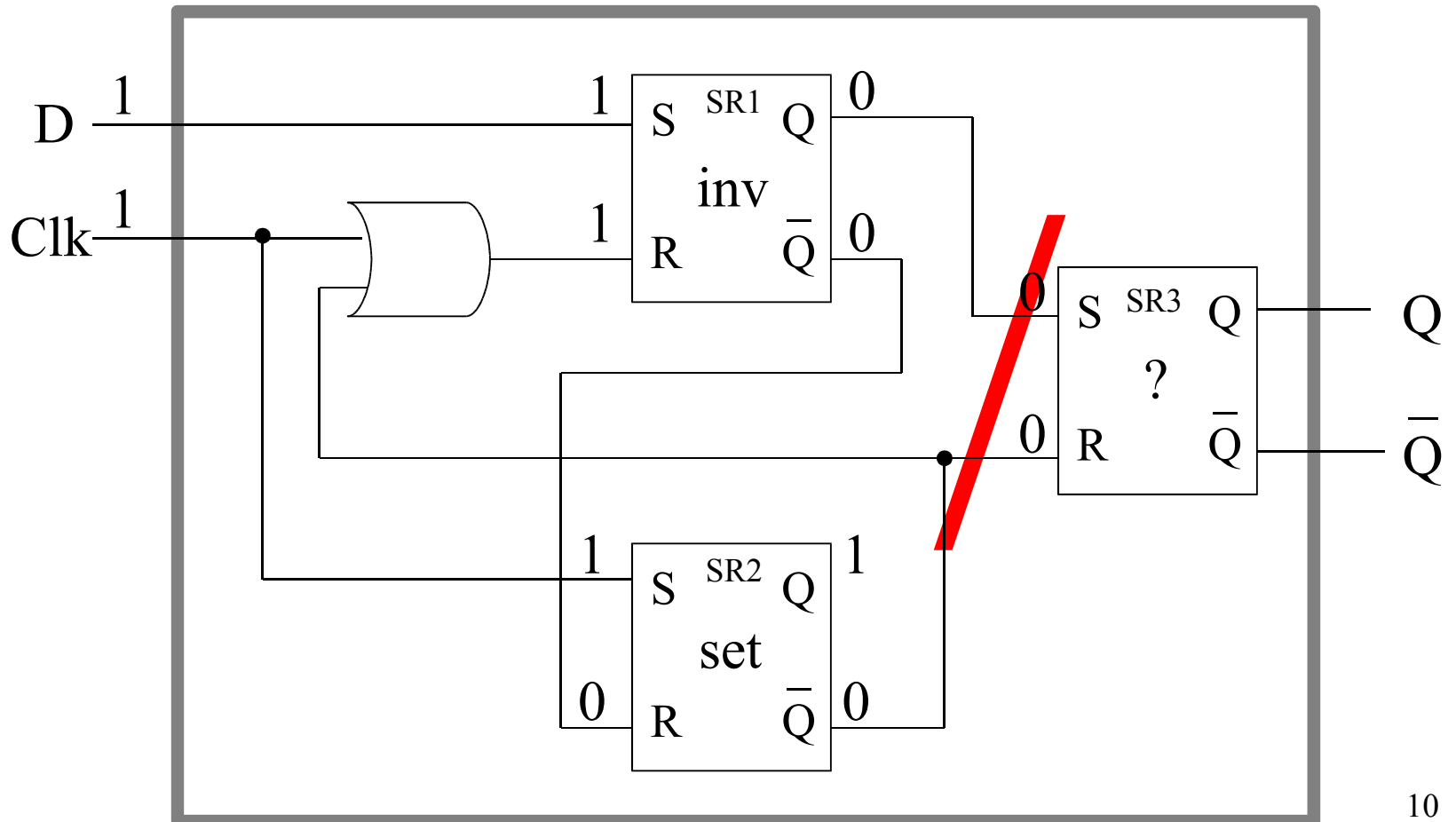


The edge-triggered D flip-flop

Case 1+: Clock = 0

SR1: valid, 1 SR3: set


Clock down Data = 1

SR2: prev, 1

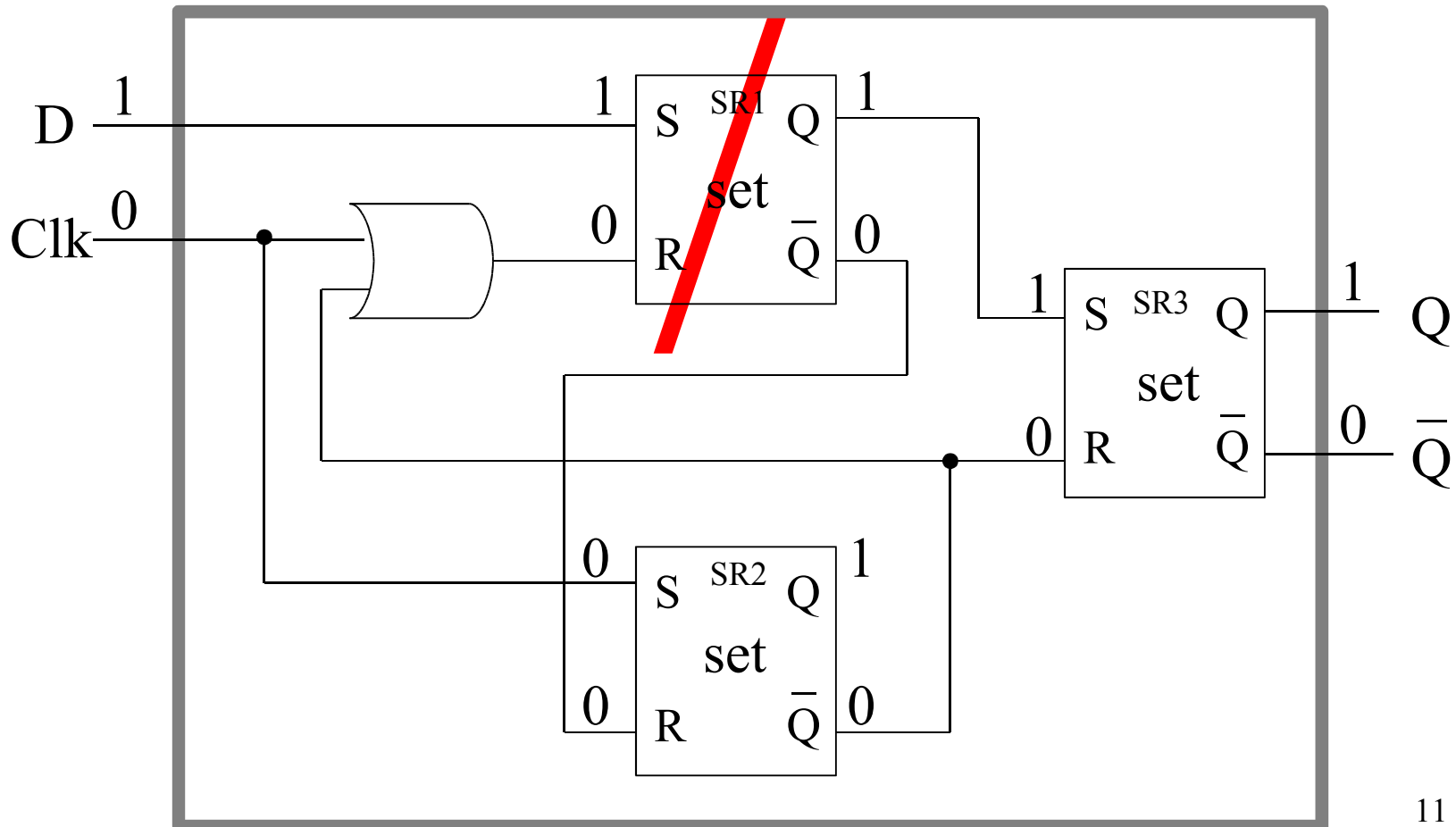


Master-slave vs. edge-triggered

Edge-triggered

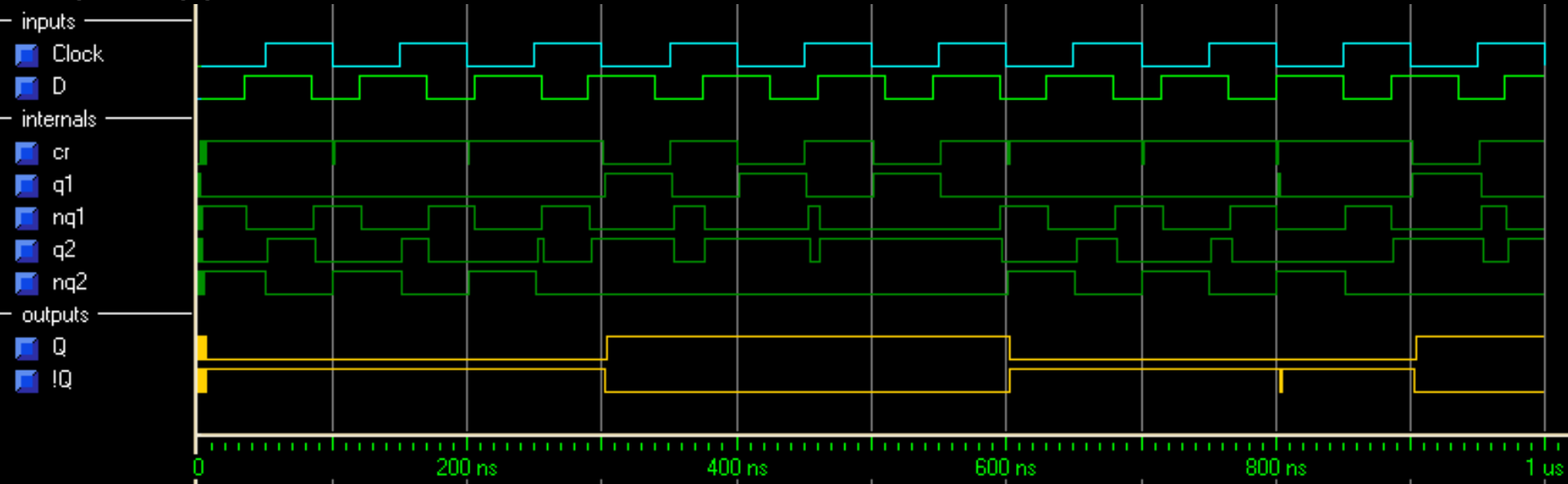

Master-slave

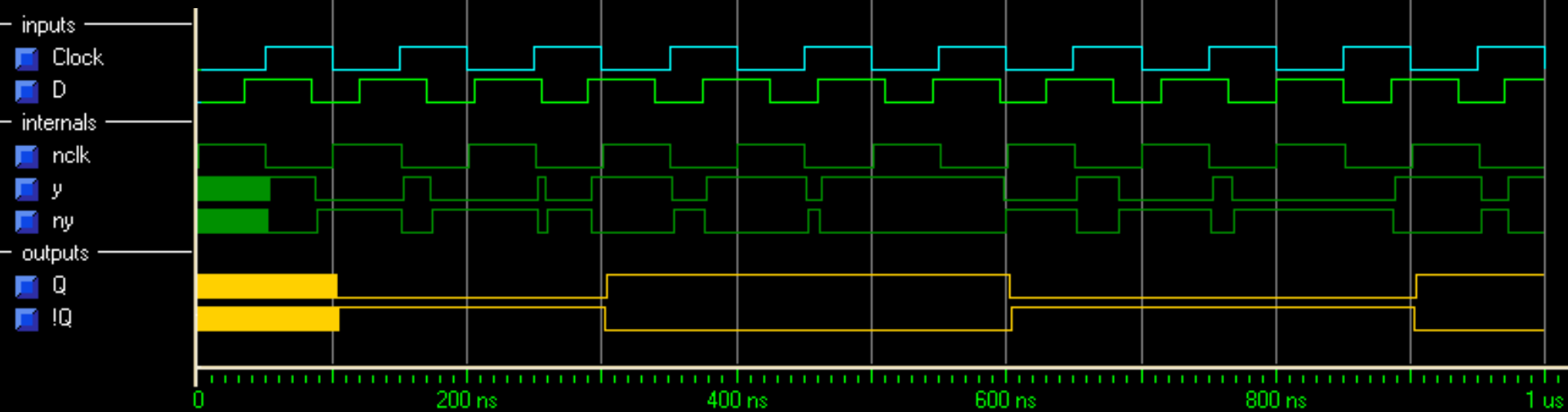

Master-slave vs. edge-triggered: conclusions


The master-slave and the edge-triggered flip-flops
are externally **IDENTICAL!**

Both sample the input signals at clock negative edge,
and make it available at output.

Forget fig. 15, page 84.

Do-it-yourself logic simulation

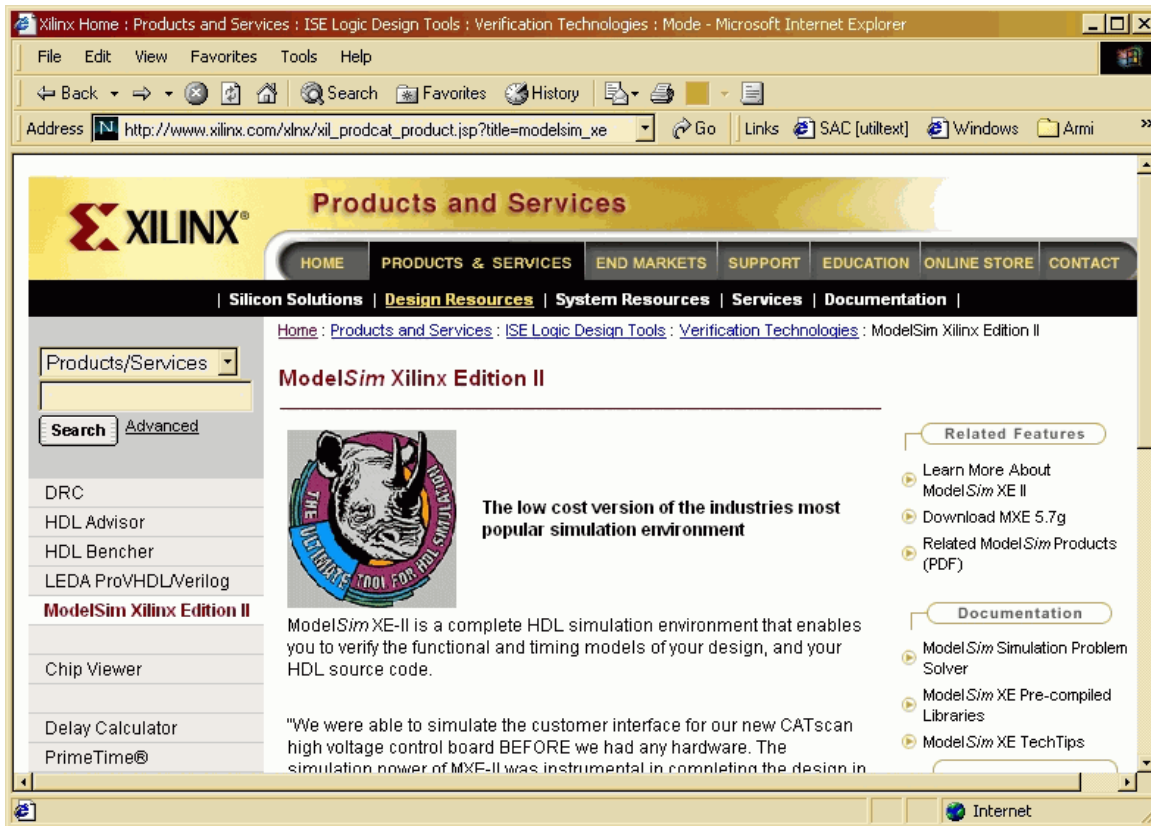1. Download MXE: “Modelsim Xilinx Edition” at:
www.xilinx.com/xlnx/xil_prodcat_product.jsp?title=modelsim_xe
2. During installation request a free license;



3. Download
scarpaz.vhd
scarpaz.tcl
and copy in dir:
examples
4. Type:
source scarpaz.tcl
init

dff
dffet3